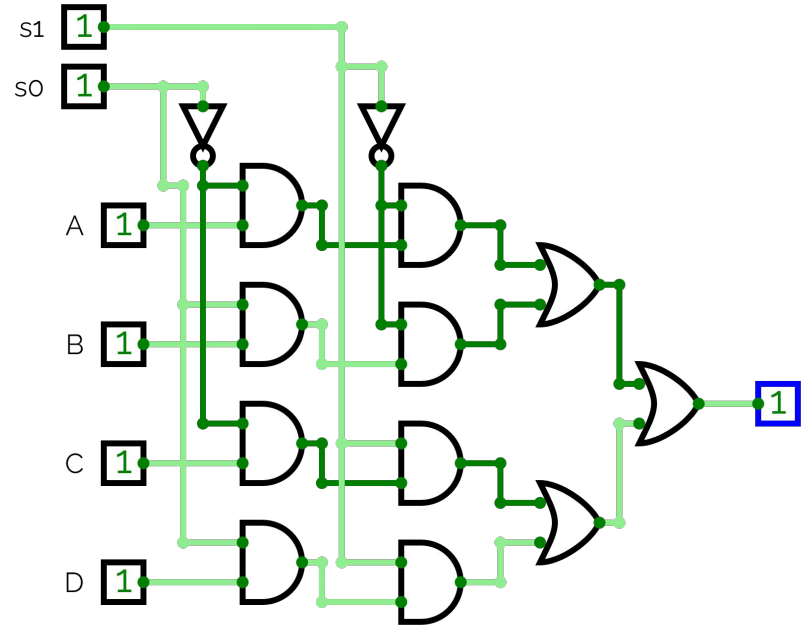


Recitation 12

Computer Architecture (section 1)

Combinatorial Circuits


- An arrangement of electronic components that perform operations on a set of inputs.
- Combinatorial logic is:
 - Time invariant
 - No memory
 - Composed of *logic gates*



Basic Logic Gates

- Common logic gates are:
NOT, AND, OR, NAND, NOR, XOR.
- These gates can be combined together to form a logic circuit.
- Boolean algebra is a theoretical framework used to analyze logic circuits.


NOT Gate

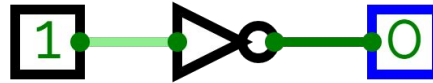

NOT Gate




NOT Gate

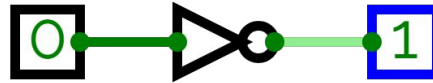


*Truth
Table*

In A	Out B
0	1
1	0


AND Gate

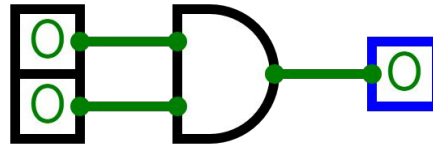


AND Gate

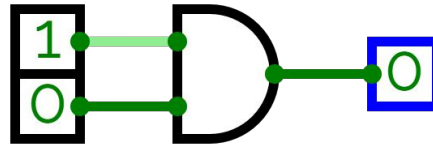

AND Gate

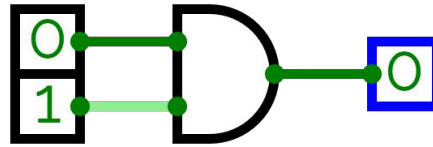

AND Gate

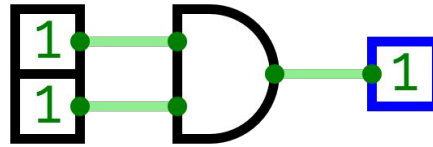


Truth


Table

In A	In B	Out C
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate

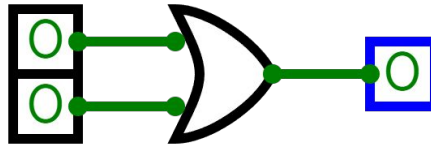


OR Gate

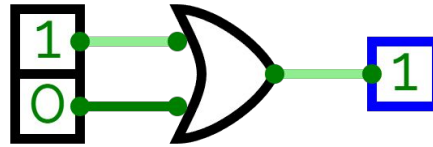

OR Gate

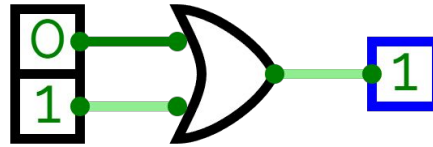


OR Gate

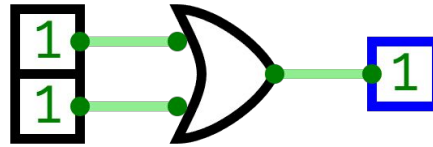


*Truth
Table*

In A	In B	Out C
0	0	0
0	1	1
1	0	1
1	1	1


NAND Gate

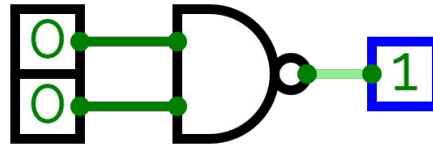


NAND Gate

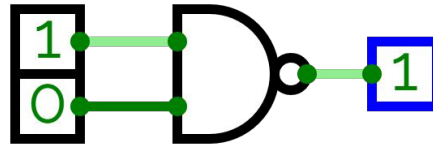

NAND Gate

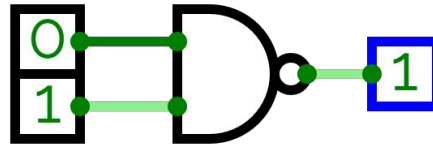


NAND Gate

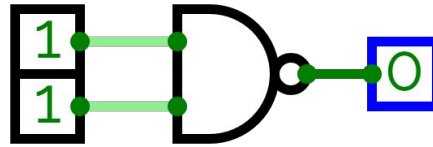


*Truth
Table*

In A	In B	Out C
0	0	1
0	1	1
1	0	1
1	1	0


NOR Gate

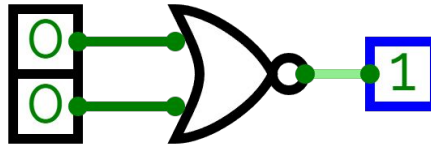


NOR Gate

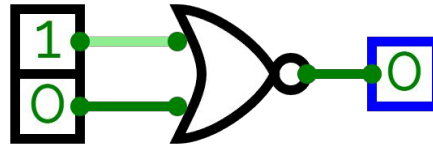

NOR Gate

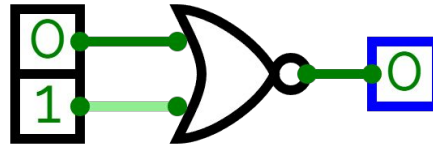

NOR Gate

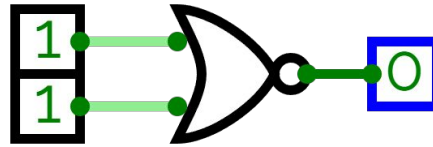


Truth


Table

In A	In B	Out C
0	0	1
0	1	0
1	0	0
1	1	0


XOR Gate

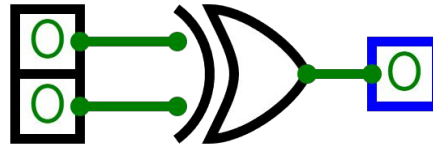


XOR Gate

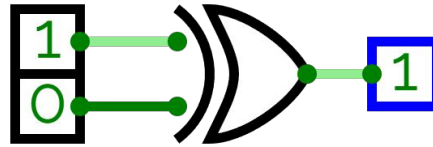

XOR Gate

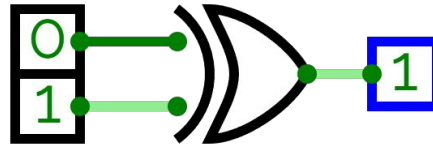

XOR Gate

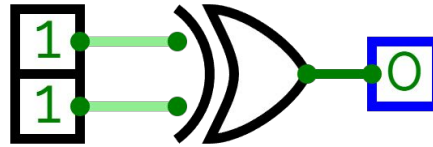


*Truth
Table*


In A	In B	Out C
0	0	0
0	1	1
1	0	1
1	1	0

Decoder

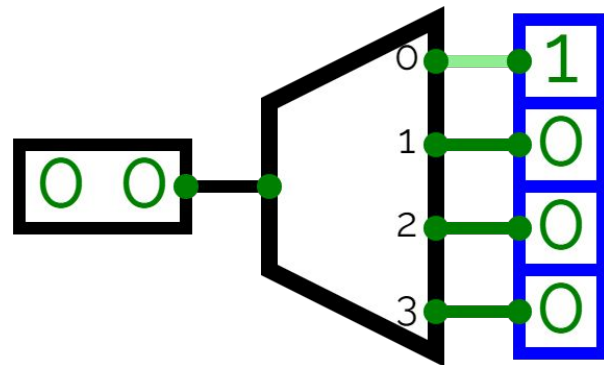
- A logic circuit with n inputs and 2^n outputs.
- Used to select the index of the represented binary input.
- Only one output bit can be set for any input.




Decoder

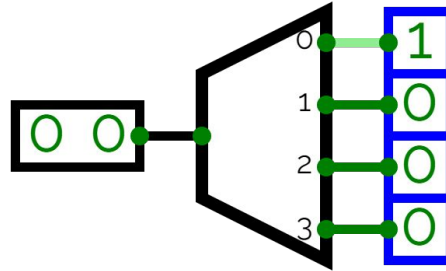


Decoder

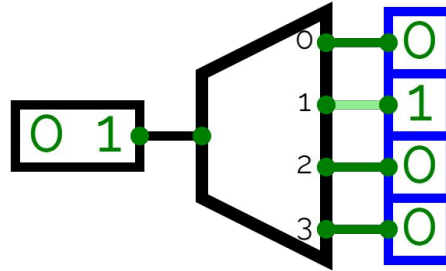

Decoder

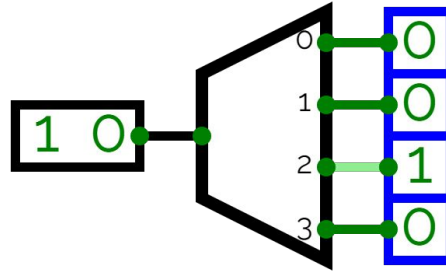


Decoder

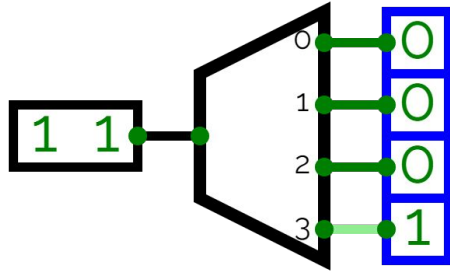


*Truth
Table*

In A	In B	Out C	Out D	Out E	Out F
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


Building a 2-bit Decoder

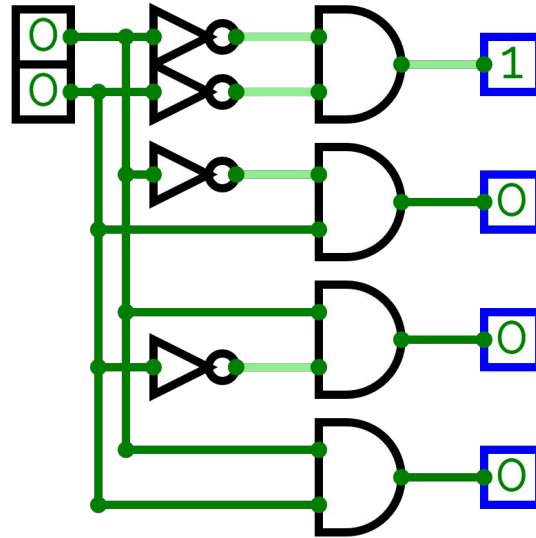


Building a 2-bit Decoder

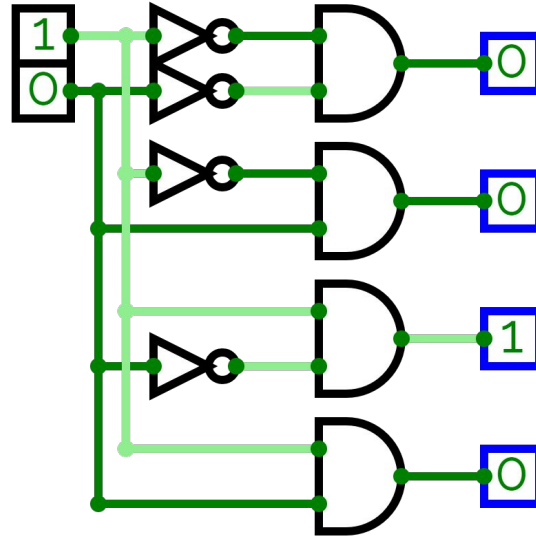

Building a 2-bit Decoder

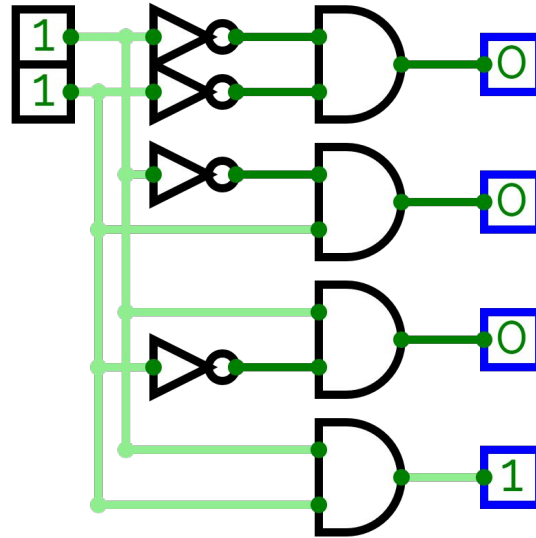

Building a 2-bit Decoder

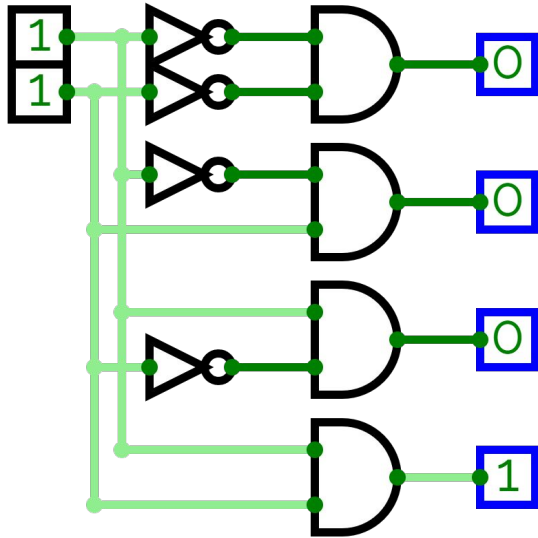


*Truth
Table*

In A	In B	Out C	Out D	Out E	Out F
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Building a 2-bit Decoder


Try it out yourself

<https://circuitverse.org/simulator>

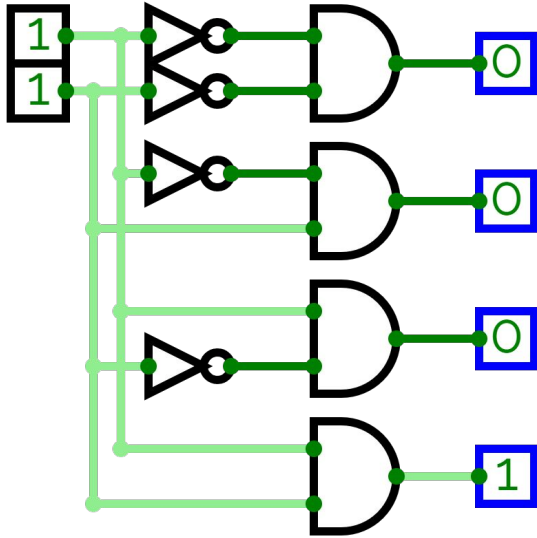


Multiplexer

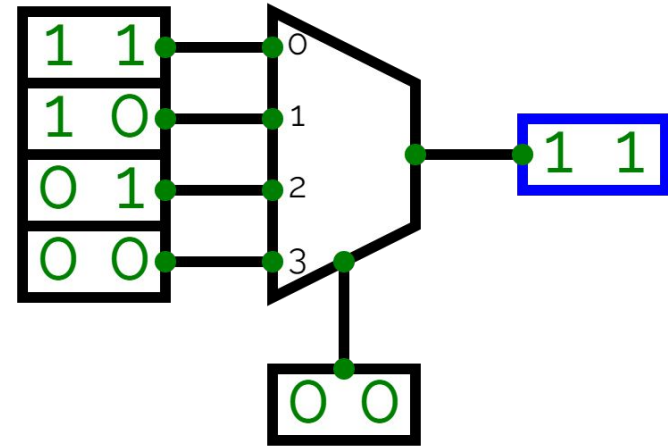
- A logic circuit with 2^n signal inputs, n select inputs, and 1 signal output .
- Used to select which signal to output.
- Output is always one of the inputs.




Multiplexer

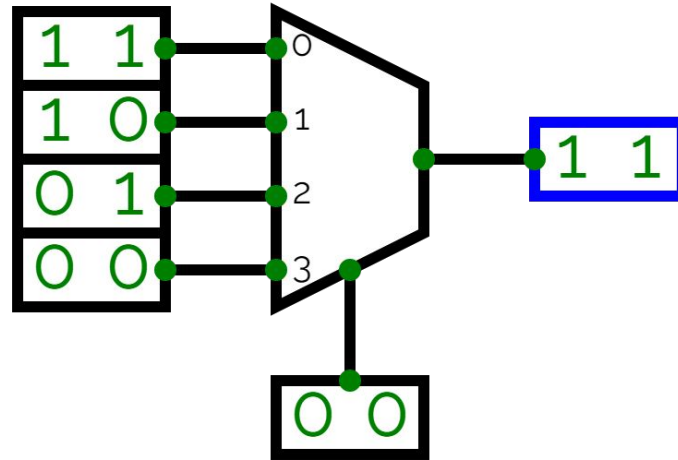


Multiplexer

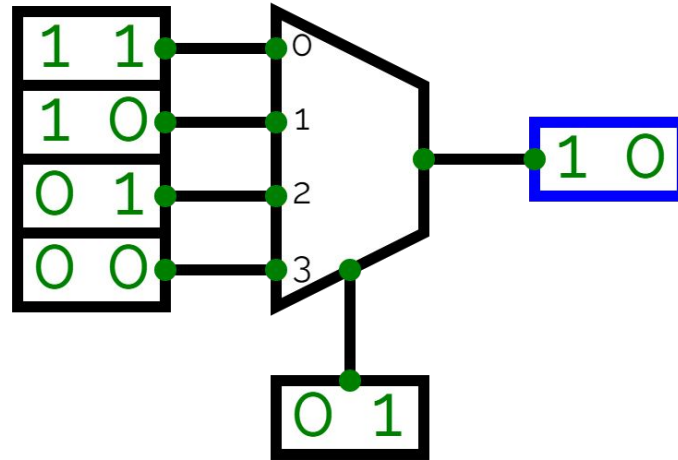


Multiplexer

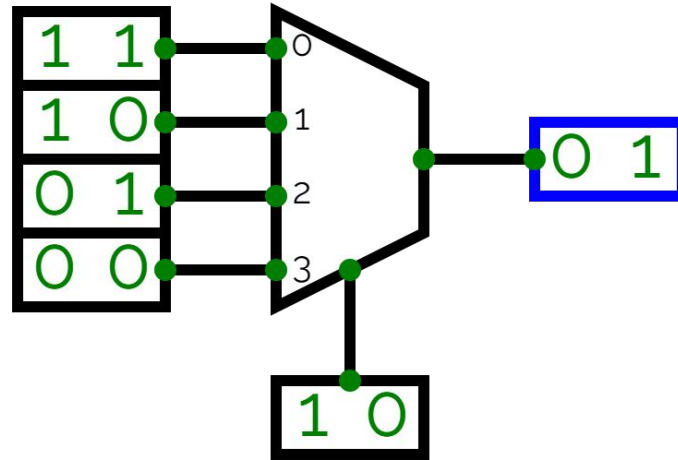


Multiplexer

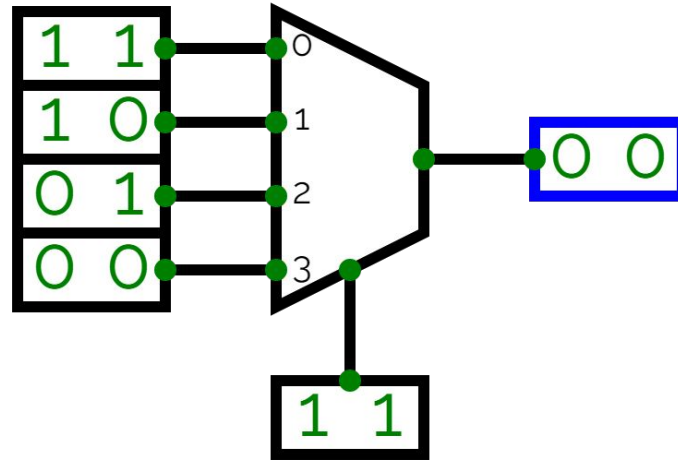


Building a 4-to-1 Multiplexer

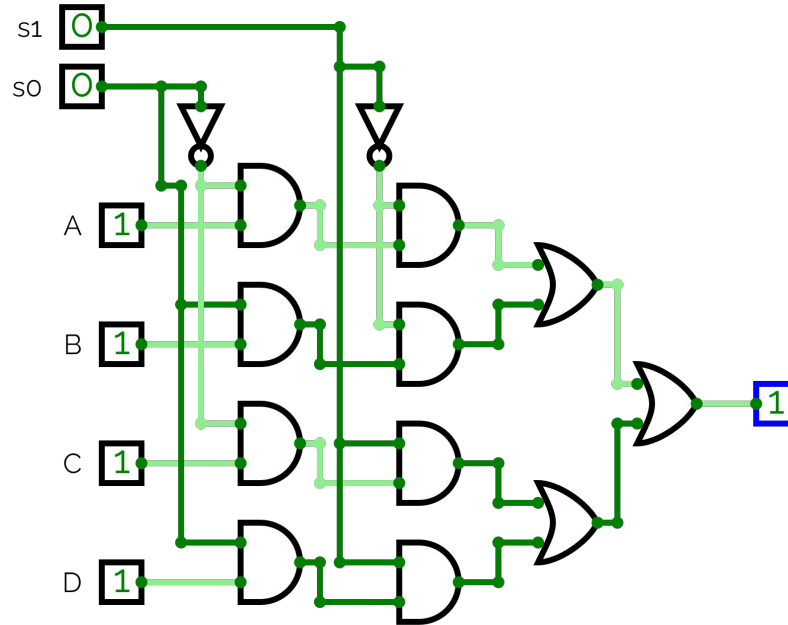


Building a 4-to-1 Multiplexer

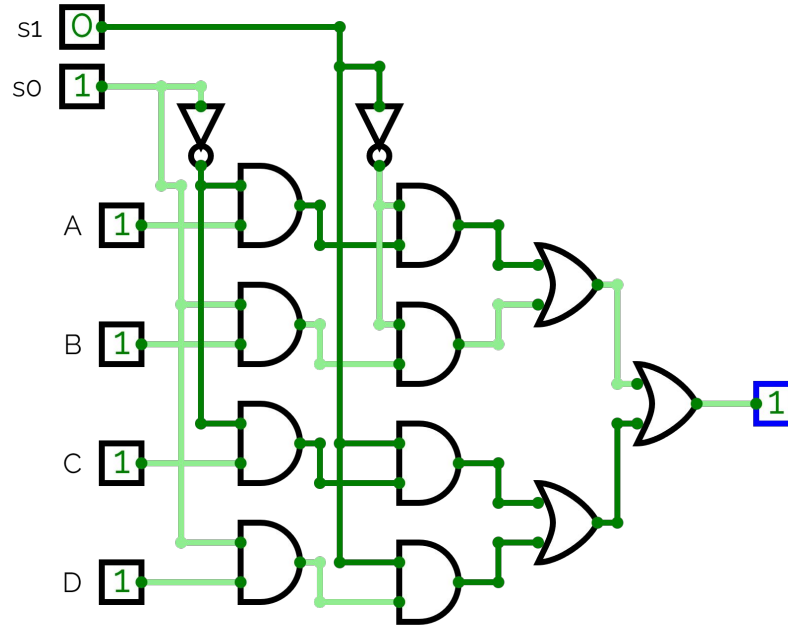

Building a 4-to-1 Multiplexer

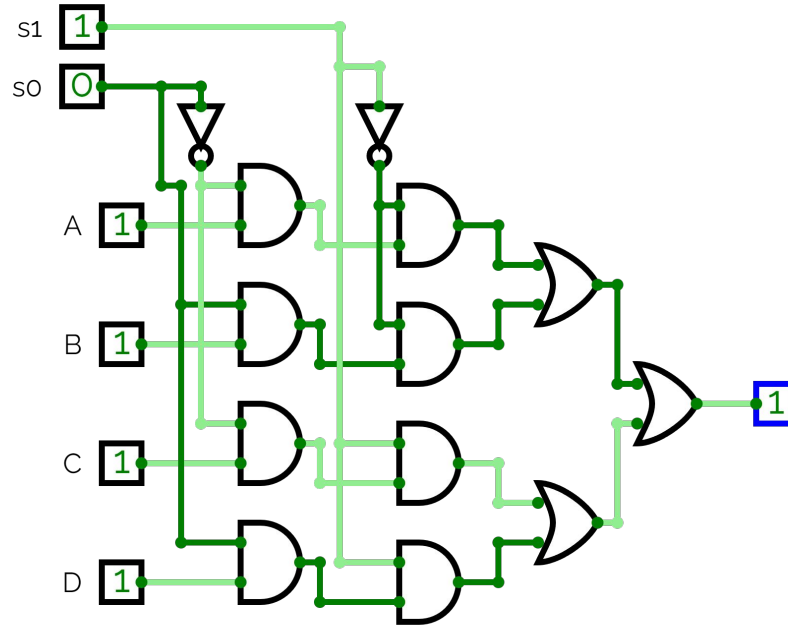


Building a 4-to-1 Multiplexer

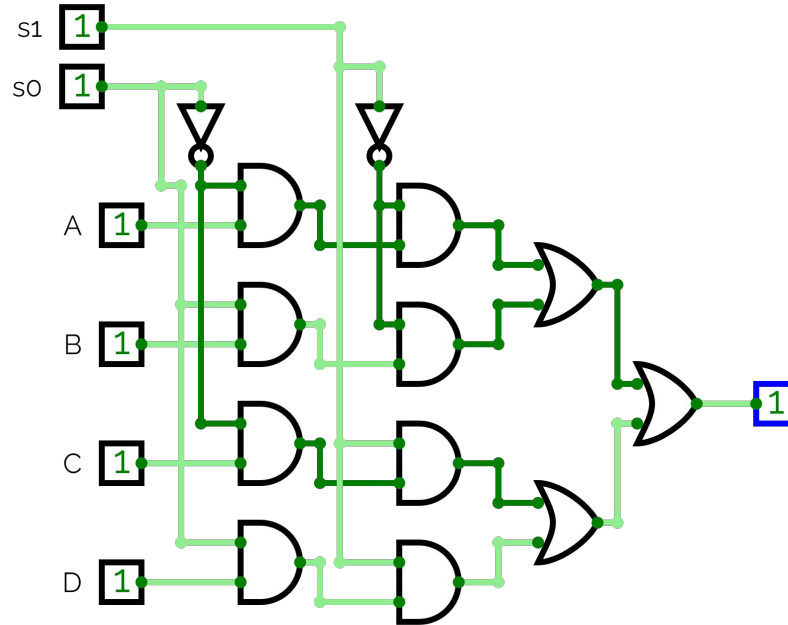

Boolean Algebra

We can define logic circuits with boolean algebra.

$$F = A\bar{C} + BC$$

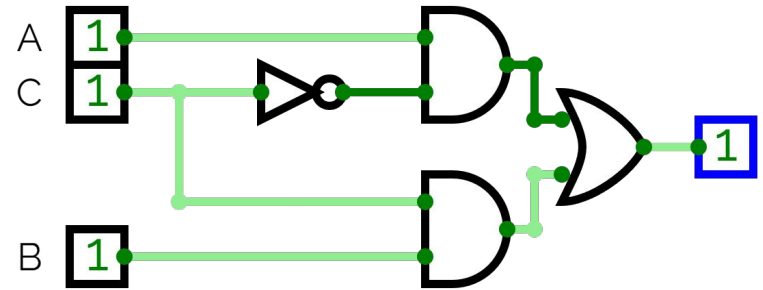

Boolean Algebra Identities

1.	Law of Identity	$A = A$ $\overline{\overline{A}} = A$
2.	Commutative Law	$A \cdot B = B \cdot A$ $A + B = B + A$
3.	Associative Law	$A \cdot (B \cdot C) = A \cdot B \cdot C$ $A + (B + C) = A + B + C$
4.	Idempotent Law	$A \cdot A = A$ $A + A = A$
5.	Double Negative Law	$\overline{\overline{A}} = A$
6.	Complementary Law	$A \cdot \overline{A} = 0$ $A + \overline{A} = 1$
7.	Law of Intersection	$A \cdot 1 = A$ $A \cdot 0 = 0$
8.	Law of Union	$A + 1 = 1$ $A + 0 = A$
9.	DeMorgan's Theorem	$\overline{AB} = \overline{A} + \overline{B}$ $\overline{A + B} = \overline{A} \cdot \overline{B}$
10.	Distributive Law	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ $A + (BC) = (A + B) \cdot (A + C)$
11.	Law of Absorption	$A \cdot (A + B) = A$ $A + (AB) = A$
12.	Law of Common Identities	$A \cdot (\overline{A} + B) = AB$ $A + (\overline{A} \cdot B) = A + B$

We can prove equality with truth tables.

De Morgan's Law

$$\overline{A B} = \overline{A} + \overline{B}$$



$$\overline{A + B} = \overline{A} \overline{B}$$



Expressing Boolean Functions

We can express boolean functions in canonical forms known and **sum-of-products** and **product-of-sums**.

$$\text{PoS} = (\bar{A}+B) (A+\bar{B})$$

A minterm is the product of all literals in the expression where each literal may be negated. A minterm can only output 1 for a single input.

$$\text{SoP} = \bar{A}B + A\bar{B}$$

Boolean Algebra Exercise

Convert the truth table to a boolean expression.

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Min terms

$$\bar{A}BC = 1$$

$$A\bar{B}C = 1$$

$$AB\bar{C} = 1$$

$$ABC = 1$$

Simplifying Boolean Expressions

Often times a boolean expression has an equivalent more concise form.

One way to simplify an expression is via identities.

$$\begin{array}{l}
 \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \\
 \downarrow \text{Factoring } BC \text{ out of 1}^{\text{st}} \text{ and 4}^{\text{th}} \text{ terms} \\
 BC(\bar{A} + A) + \bar{A}\bar{B}C + AB\bar{C} \\
 \downarrow \text{Applying identity } A + \bar{A} = 1 \\
 BC(1) + \bar{A}\bar{B}C + AB\bar{C} \\
 \downarrow \text{Applying identity } 1A = A \\
 BC + \bar{A}\bar{B}C + AB\bar{C} \\
 \downarrow \text{Factoring } B \text{ out of 1}^{\text{st}} \text{ and 3}^{\text{rd}} \text{ terms} \\
 B(C + \bar{A}\bar{C}) + \bar{A}\bar{B}C \\
 \downarrow \text{Applying rule } A + \bar{A}B = A + B \text{ to the } C + \bar{A}\bar{C} \text{ term} \\
 B(C + A) + \bar{A}\bar{B}C \\
 \downarrow \text{Distributing terms} \\
 BC + AB + \bar{A}\bar{B}C \\
 \downarrow \text{Factoring } A \text{ out of 2}^{\text{nd}} \text{ and 3}^{\text{rd}} \text{ terms} \\
 BC + A(B + \bar{B}C) \\
 \downarrow \text{Applying rule } A + \bar{A}B = A + B \text{ to the } B + \bar{B}C \text{ term} \\
 BC + A(B + C) \\
 \downarrow \text{Distributing terms} \\
 BC + AB + AC \\
 \text{or} \\
 AB + BC + AC
 \end{array}$$

Simplified result